

## **International Institute of Information Technology, Hyderabad**

### **Course - VLSI Design**

Date – 13/9/2019

**LAB Assignment Submission Date – 30/10/2019 (23:59 IST).**

**Late submission will not be accepted.**

#### **LAB 3.**

Design ASIC (from Verilog code till GDSII File) using Cadence and Perform full FPGA Flow( from Verilog to Dumping code into FPGAs) for the following Digital Blocks.

- a) 1 bit Full Adder: Design using Logic gates.
- b) 4 bit Carry Ripple Adder: Design using 1 bit Full adder.
- c) 16 Bit Carry Ripple Adder :  
The 16-bit adder will use 4 - bit ripple carry adders as components. The 16 – bit adder has two inputs '*a*' and '*b*' of type bit vector representing the addend and augend; and 1-bit input signal *c\_in* of type bit representing the carryin. The adder produces one output signal *s* of type bit vector representing the sum word and a 1-bit output signal *c\_out* of type bit representing the carryout.
- d) 4 bit Carry Look-Ahead (CLA)
- e) 16 bit Carry Look-Ahead :  
The 16-bit adder will use 4 - bit CLA as components. The 16 – bit adder has two inputs '*a*' and '*b*' of type bit vector representing the addend and augend; and 1-bit input signal *c\_in* of type bit representing the carryin. The adder produces one output signal *s* of type bit vector representing the sum word and a 1-bit output signal *c\_out* of type bit representing the carryout.

Write Verilog code and test benches for the above digital blocks.

Submit the following inside a folder from Cadence:

- 1) Verilog code and Test bench.
- 2) All reports generated by genus: area, power, timing and netlist.
- 3) Innovus : Area, Power and Timing report (pre-place, post-rout, and sign-off).
- 4) Submit Snapshots: Timing Diagram (from NC launch), RTL schematic (from Genus) and Physical Design (from Innovus).

Make a report and write Truth table and Boolean expression of the output for the 2 bit Full adder. Also draw its logic diagram.

Make a comparison report which will compare the area, power and delay (Find the delay of the ripple carry adder using the waveform you got from the simulation) obtained for all the above digital blocks. If possible provide reasons also.

FOR XILINX ISE -

1. Submit verilog code for main code, testbench and .ucf(implementation constraints file) file.
2. Submit the following snapshots from Xilinx ISE:
  - a) Timing Diagram depicting clearly all possible combinations of test inputs
  - b) RTL schematic depicting all logic gates present in the logic design
3. Also report Area, Power and Delay of your design.

**Note: Submit reports in separate folder for each Digital Block.**

**Please make sure you don't do it in the last day because the speed of server gets slow as everybody tries to access it. So start doing it from the first day and request regarding extension of deadline because of slowdown of servers won't be accepted.**

For learning Verilog and writing its test bench you can refer to the following website:

**[www.asic-world.com](http://www.asic-world.com)**

**How to submit your assignment:**

1. Make a folder and rename it to your name\_roll no and put rest of the folders inside it.
3. Compress that folder into .tar file and submit that folder in moodle.

**NOTE:** Cheating your LAB assignments from your friends is strictly prohibited though a group discussion is appreciated. Please make acknowledgements in your report if you have taken help from your friends.

If plagiarism (copying code) found strict action will be taken against you.

**All The Best!!! ☺**